

Chapter 7

Deep Understanding of Verilog HDL

Two Types of Assignment Statements in Process

⌘ Blocking Assignment with Unspecified Time-delay

target variable name=drive expression;

Two Types of Assignment Statements in Process

⌘ Blocking Assignment with Specified Time-delay

*[delay] target variable name=drive
expression;*

target variable name= [delay] drive expression;

```
... //procedural statement  
    Y1 = A^B;  
#6 Y2 = A & B | C;
```

```
... /procedural statement  
Y1 = A^D;  
Y2 = #6 A & E | C;
```

<pre>assign Q1 = A B; assign Q1 = B&C; assign Q1 = ~C;</pre>	<pre>begin Q1 = A B; Q1 = B&C; Q1 = ~C ; end</pre>	<pre>begin Q1 <= A B; Q1 <= B&C; Q1 <= ~C ; end</pre>
--	--	--

<pre>assign Q1 = A B; assign Q1 = B&C; assign Q1 = ~C;</pre>	<pre>begin Q1 = A B; Q1 = B&C; Q1 = ~C ; end</pre>	<pre>begin Q1 <= A B; Q1 <= B&C; Q1 <= ~C ; end</pre>
--	--	--

```
begin
Y1 = #6 A^B;
Y2 = #4 A|B;
Y3 = #7 A&B;
end
```

```
begin
Y1 <= #6 A^B;
Y2 <= #4 A|B;
Y3 <= #7 A&B;
end
```

```
begin
Y1 = #5 A^B;
Y2 <= #3 A|B;
Y3 <= #2 A&B;
Y4 = #4 (~B); end
```

```
module DDF3 (CLK, D, Q);  
input CLK, D; output Q; reg a, b, Q;  
always @(posedge CLK) begin  
a <= D;  
b <= a;  
Q <= b; end  
endmodule
```

```
module DFF3 (CLK, D, Q);  
input CLK, D; output Q; reg a, b, Q;  
always @(posedge CLK) begin  
a = D;  
b = a;  
Q = b; end  
endmodule
```

 


Figure: The RTL diagram of Example 7-11 after synthesis

 


Figure: The RTL diagram of Example 7-12 after synthesis

Further Discussion of Different Initialization Ways

```
module MUX41a(D,S,DOUT);
  output DOUT ;
  input [3:0] D; input [1:0] S;
  integer T; reg DOUT;
  always @(D,S)
  begin  T <= 0;
    if (S[0]==1) T<=T+1;
    if (S[1]==1) T<=T+2;
    case (T)
      0 : DOUT = D[0] ;
      1 : DOUT = D[1] ;
      2 : DOUT = D[2] ;
      3 : DOUT = D[3] ;
      default : DOUT = D[0] ;
    endcase  end
endmodule
```

```
module MUX41a(D,S,DOUT);
  output DOUT ;
  input [3:0] D; input [1:0] S;
  integer T; reg DOUT;
  always @(D,S)
  begin  T = 0;
    if (S[0]==1) T=T+1;
    if (S[1]==1) T=T+2;
    case (T)
      0 : DOUT = D[0] ;
      1 : DOUT = D[1] ;
      2 : DOUT = D[2] ;
      3 : DOUT = D[3] ;
      default : DOUT = D[0] ;
    endcase  end
endmodule
```

 



Figure: The operational timing of Example 7-13

 


Figure: The operational timing of Example 7-14

Discussion of Procedural Statement

```

module mux2_1
  (CLK, D, Q, RST);
  output Q;
  input CLK,D,RST;
  reg Q;
  always @(D, CLK, RST)
  if(CLK) Q <= D;
  else Q <= RST;
endmodule
  
```

```

module COMP(A,B,Q);
  input[3:0] A,B;
  output Q; reg Q;
  always @(A,B)
  begin
    if(A>B) Q=1'b1;
    else
    if(A<B) Q=1'b0;
  end
end module
  
```

```

module COMP(A,B,Q);
  input[3:0] A,B;
  output Q; reg Q;
  always @(A,B)
  begin
    if(A>B) Q=1'b1;
    else if(A<B) Q=1'b0;
    else Q=1'bz;
  end
end module
  
```

 


Figure: The RTL diagram of example 7-15

 


Figure: The RTL diagram of Example 7-16, and the output port is added by latch.

 


Figure 7-7 The circuit of Example 7-17, which is a pure combinational circuit.

Design of Three-state and Bidirectional Port

```

module tri4B (ENA, DIN, DOUT);
    input ENA;
    input [3:0] DIN ;
    output [3:0] DOUT ;
    reg [3:0] DOUT;
    always @(DIN, ENA)
        if (ENA)    DOUT <= DIN ;
        else       DOUT <= 4'HZ;
endmodule

```

 


Figure: 4-bit three-state control gate circuit

```

module bi4b( TRI_PORT, DOUT, DIN, ENA, CTRL );
  inout TRI_PORT;    input  DIN, ENA, CTRL;
  output DOUT ;
  assign TRI_PORT = ENA ? DIN : 1'bz;
  assign DOUT = TRI_PORT | CTRL;
endmodule

```

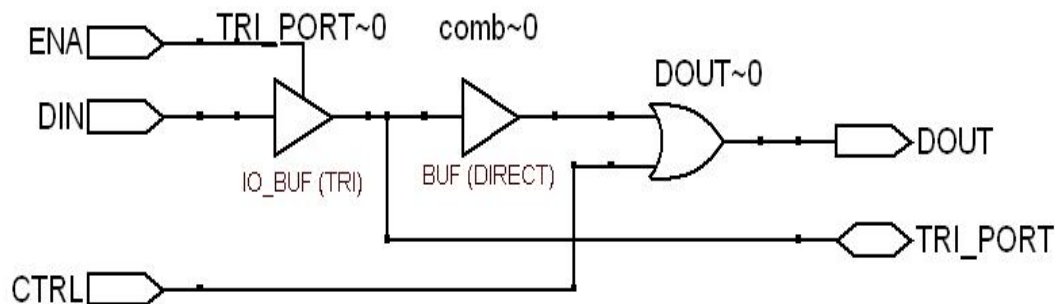


Figure: The RTL diagram of circuit design of 1-bit bidirectional port in Example 7-19

```

module BI4B(CTRL,DIN,Q,DOUT);
input CTRL;  input[3:0] DIN;
inout[3:0]Q; output[3:0] DOUT;
reg [3:0] DOUT,Q ;
always @(Q,DIN,CTRL)
  if (!CTRL) DOUT<=Q ;
  else
begin Q<=DIN; DOUT<=4'HZ; end
endmodule

```

```

module BI4B(CTRL,DIN,Q,DOUT);
input CTRL;  input[3:0] DIN;
inout[3:0] Q; output[3:0] DOUT;
reg [3:0] DOUT,Q ;
always @(Q,DIN,CTRL)
if (!CTRL) begin DOUT<=Q;
              Q<=4'HZ; end else
begin Q<=DIN; DOUT<=4'HZ; end
endmodule

```

 


Figure: The simulation waveform of Example 7-20

 


Figure: The simulation waveform of Example 7-21

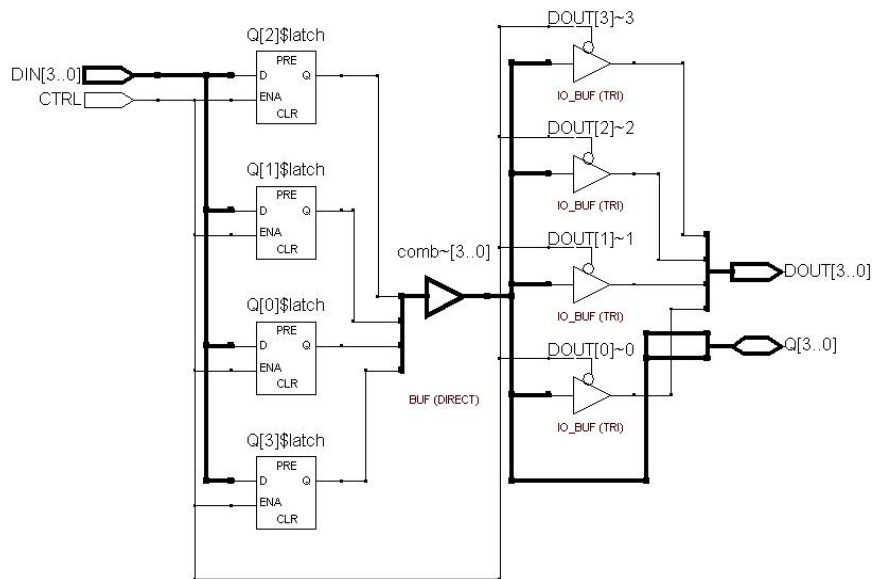


Figure: The RTL diagram of Example 7-20

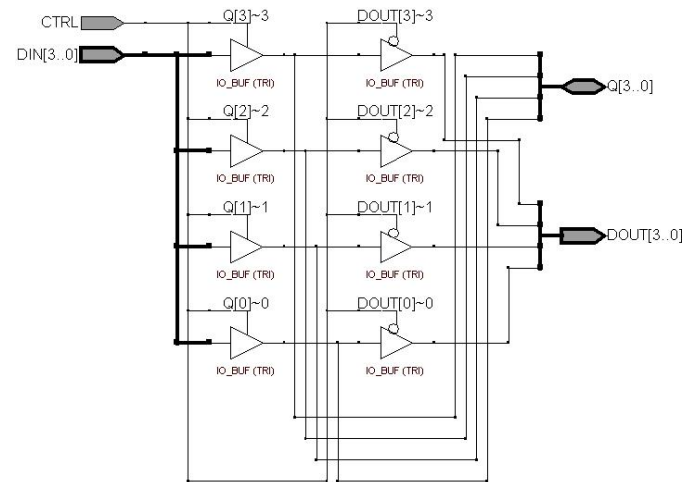


Figure: The RTL diagram of Example 7-21

Design of Three-state Bus Control Circuit

```
module triBUS4(
  IN3,IN2,IN1,IN0,ENA,DOUT);
  input[3:0] IN3,IN2,IN1,IN0 ;
  input[1:0] ENA;
  output[3:0] DOUT;
  reg[3:0] DOUT;
  always @(ENA,IN3,IN2,IN1,IN0)
  begin
    if (ENA==0) DOUT=IN3 ;
    else DOUT=4'HZ;
    if (ENA==1) DOUT=IN2 ;
    else DOUT=4'HZ;
    if (ENA==2) DOUT=IN1 ;
    else DOUT=4'HZ;
    if (ENA==3) DOUT=IN0 ;
    else DOUT=4'HZ;
  end
endmodule
```

```
module triBUS4(
  IN3,IN2,IN1,IN0,ENA,DOUT);
  input[3:0] IN3,IN2,IN1,IN0 ;
  input[1:0] ENA;
  output[3:0] DOUT; reg[3:0]DOUT;
  always @(ENA, IN0)
  if (ENA==2'b00) DOUT=IN0;
  else DOUT=4'hz;
  always @(ENA, IN1)
  if (ENA==2'b01) DOUT=IN1;
  else DOUT=4'hz;
  always @(ENA, IN2)
  if (ENA==2'b10) DOUT=IN2;
  else DOUT=4'hz;
  always @(ENA, IN3)
  if (ENA==2'b11) DOUT=IN3;
  else DOUT=4'hz;
endmodule
```

 


Figure: The RTL diagram of Example 7-22

 


Figure: The 2-bit simplified RTL diagram of Example 7-23

Resource Sharing

```
module multmux (A0, A1, B, S, R);  
  input[3:0] A0, A1, B; input S;  
  output[7:0] R; reg[7:0] R;  
  always @(A0 or A1 or B or S)  
  begin  
    if (S==1'b0) R <= A0*B;  
    else R <= A1*B; end  
endmodule
```

```
module multmux (A0, A1, B, S,R);  
  input[3:0] A0, A1, B; input S;  
  output[7:0] R; wire [7:0] R;  
  reg [3:0] TEMP;  
  always @(A0 or A1 or B or S)  
  begin if (S==1'b0) TEMP<=A0;  
    else TEMP <= A1; end  
  assign R = TEMP*B;  
endmodule
```

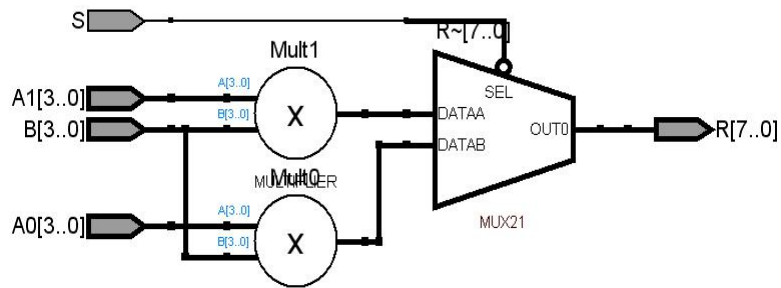


Figure: The RTL structure of first multiplication and next selection design method

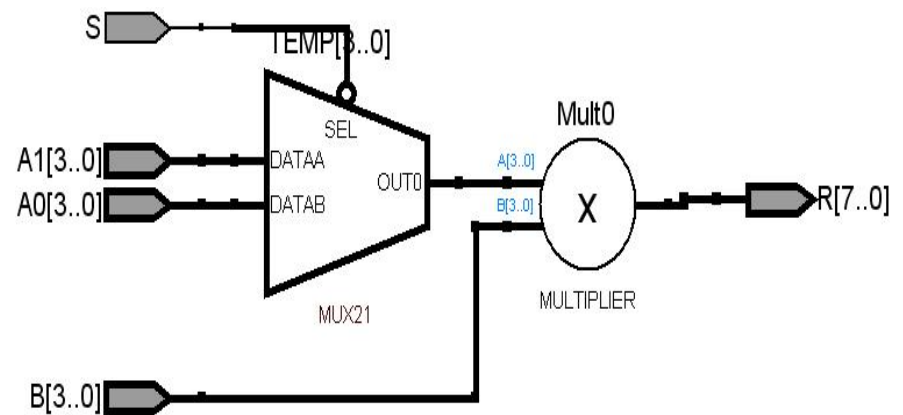


Figure: The RTL structure of first selection and next multiplication design method

Logic Optimization

In the practical design, we always meet the case that two numbers multiply with each other and one of them is a constant.

```
module mult1 (clk, ma, mc);  
  input clk; input[11:0] ma;  
  output[23:0] mc;  
  reg[23:0] mc; reg[11:0] ta,tb;  
  always @(posedge clk)  
  begin ta<=ma; mc<=ta * tb;  
    tb <= 12'b100110111001; end  
endmodule
```

```
module mult2 (clk, ma, mc);  
  input clk; input[11:0] ma;  
  output[23:0] mc;  
  reg[23:0] mc; reg[11:0] ta;  
  parameter tb=12'b100110111001;  
  always @(posedge clk)  
  begin ta<=ma ; mc<=ta * tb; end  
endmodule
```

If it is adapted to the EPF10K20, the example of 9-3 totally consumes LC of 167 and the example of 9-4 consumes LC of 93.

Serialization

$$\text{yout} = a_0b_0 + a_1b_1 + a_2b_2 + a_3b_3$$

[Example]

```
module pmultadd (clk, a0, a1, a2, a3, b0, b1, b2, b3, yout);  
    input clk;    input[7:0] a0, a1, a2, a3, b0, b1, b2, b3;  
    output[15:0] yout;    reg[15:0] yout;  
    always @(posedge clk) begin  
        yout <= ((a0 * b0)+(a1 * b1))+((a2 * b2)+(a3 * b3)) ;    end  
endmodule
```

It totally consumes 4 8-bit multiplier and some adder. If it is adapted to EP3C5, 460 LC will be consumed.

The serialization is to (1) split up the parallel execution logic which consumes large resource and complete within one clock period; (2) extract the same logic module; (3) multiplex the logic module in time and finish the same functionality by using several clock periods. The drawback of this method is the lowering of the operation speed.

[Example]

```

module smultadd (clk, start, a0, a1, a2, a3, b0, b1, b2, b3, yout);
    input clk, start; input[7:0] a0, a1, a2, a3, b0, b1, b2, b3;
    output[15:0] yout; reg[15:0] yout, ytmp; reg[2:0] cnt;
    wire[7:0] tmpa, tmpb; wire[15:0] tmp;
    assign tmpa=(cnt==0)? a0:(cnt==1)? a1:(cnt==2)? a2:(cnt==3)? a3:a0;
    assign tmpb=(cnt==0)? b0:(cnt==1)? b1:(cnt==2)? b2:(cnt==3)? b3:b0;
    assign tmp = tmpa * tmpb ;
    always @(posedge clk) begin
        if (start==1'b1) begin cnt<=3'b000 ; ytmp<={16{1'b0}} ; end
        else if (cnt<4) begin cnt<=cnt+1 ; ytmp<=ytmp+tmp ; end
        else if (cnt==4) begin yout<=ytmp ; end end
    endmodule

```

It only needs one 8-bit multiplier and one 16-bit adder. Moreover, 3-bit binary counter and tow large selector are needed. If the same synthesis/adaption configuration is used, 186 LC will be consumed.

Speed optimization



The design of pipeline

The pipeline technology is one of the most commonly used technologies in the speed optimization. It can significantly enhance the upper limit of the operational speed of the circuit design.

In fact, adding the pipeline into the design will not reduce the delay of the design. Sometimes, it will a little bit increase the delay of the inserted register. However, it will enhance the overall operation speed.

Speed Optimization

 


Figure: The unuse of pipeline

$$T_a \leq T_{CLK} \Rightarrow \frac{1}{T_a} \geq \frac{1}{T_{CLK}} = f_{CLK}$$

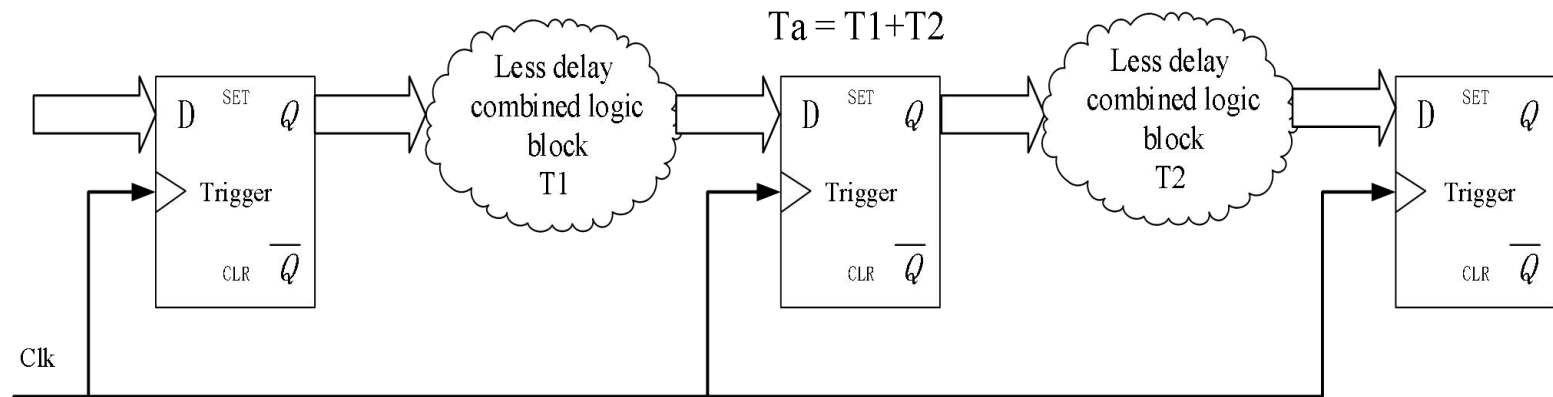


Figure: The use of pipeline structure

$$F_{\max} \approx F_{\max 1} \approx F_{\max 2} \approx 1 / T_1$$

$$T_1 \leq T_{CLK} \Rightarrow \frac{1}{T_1} \geq \frac{1}{T_{CLK}} \Rightarrow \frac{2}{T_a} \geq \frac{1}{T_{CLK}} = f_{CLK}$$

 


Figure: The working diagram of pipeline

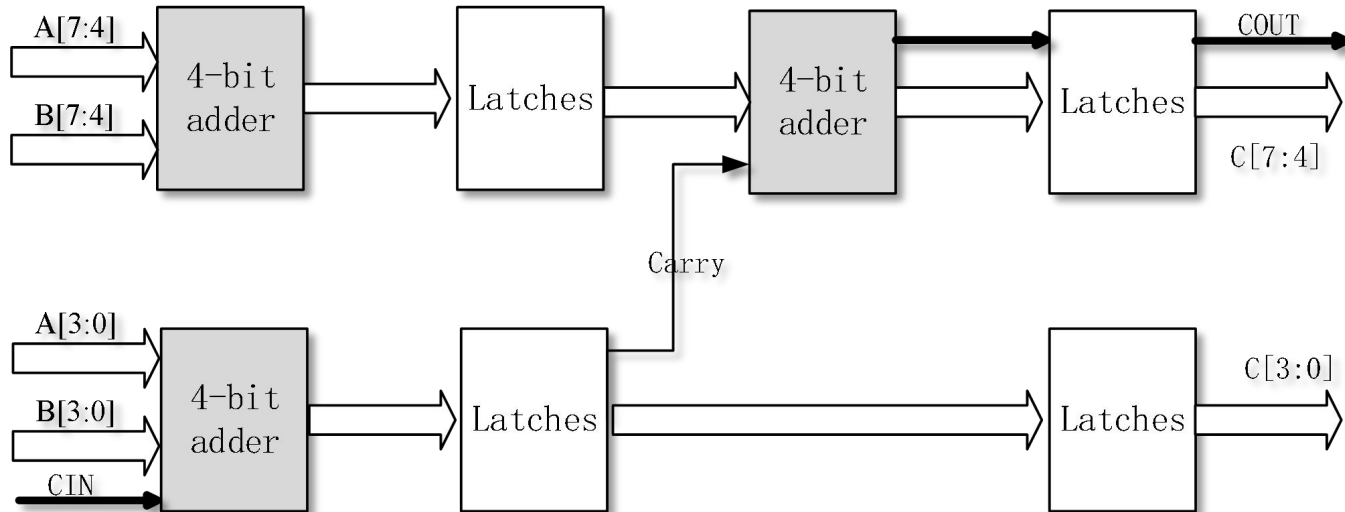


Figure: The working diagram of 8-bit adder pipeline

 


Figure: The timing simulation waveform of Example 7-30

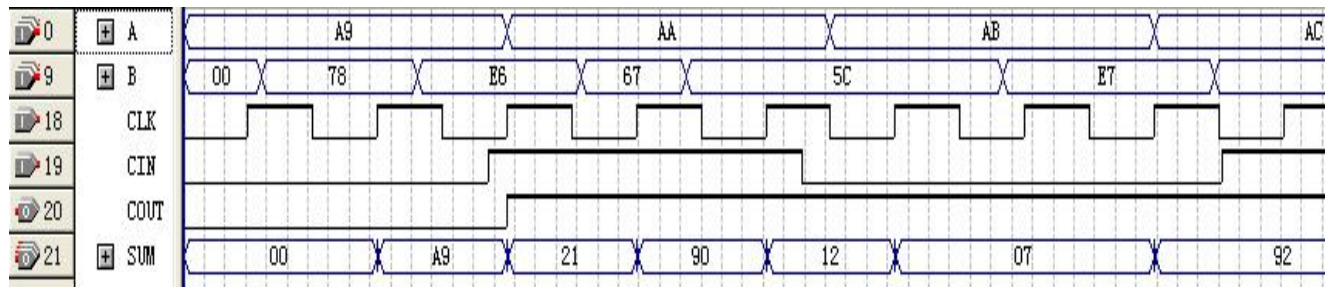


Figure: The timing simulation waveform of Example 7-31

[**Example**] Ordinary adder, and the synthesis result of EP3C10: LCs=10, REG=0,
T=7.748ns

```
module ADDER8 (CLK, SUM, A, B, COUT, CIN);  
    input [7:0] A, B; input CLK, CIN; output COUT; output [7:0] SUM;  
    reg COUT; reg [7:0] SUM;  
    always @(posedge CLK) {COUT, SUM[7:0]} <= A+B+CIN;  
endmodule
```

[**Example**] Pipelining adder, and the synthesis result of EP3C10: T=3.63ns, LCs=24, REG=22

```
module ADDER8 (CLK, SUM, A, B, COUT, CIN);
    input [7:0] A, B; input CLK, CIN; output COUT; output [7:0] SUM;
    reg TC, COUT; reg [3:0] TS, TA, TB; reg [7:0] SUM;
    always @(posedge CLK) begin
        {TC, TS} <= A[3:0] + B[3:0] + CIN; SUM[3:0] <= TS; end
    always @(posedge CLK) begin
        TA <= A[7:4]; TB <= B[7:4];
        {COUT, SUM[7:4]} <= TA + TB + TC; end
Endmodule
```